

B.Sc. Semester-III (Honours) Examination, 2020-21

PHYSICS

Course Id: 32413

Course Code: SH/PHS/303/C-7

Course Title: Digital Systems and Applications

Time: 1 Hour 15 Minutes

Full Marks: 25

The figures in the margin indicates full marks.

Candidates are required to give their answers in their own words as far as practicable

Section-I

1. Answer any *five* questions: 1X5=5
- i) What is 2's compliment?
 - ii) Why is a parallel counter faster than a ripple counter?
 - iii) What is an excitation table?
 - iv) What do you mean by multiplexing?
 - v) What is the use of a Karnaugh map?
 - vi) What is the difference between a synchronous and an asynchronous counter?
 - vii) Convert $(1001.0101)_2$ into its decimal equivalent.
 - viii) What do you mean by monolithic IC?

Section-II

Answer any *two* questions: 5X2=10

- 2. What is a truth table? Explain how to subtract two Boolean numbers by compliment method. 1+4
- 3. What is a multiplexer? Draw a logic block diagram of a 4:1 multiplexer. Design a 4 to 1 multiplexer using basic gates. 1+1+3
- 4. Draw the circuit diagram of a mono stable multi vibrator using IC 555 timer. Explain the operation of a mono stable multi vibrator using 555 timer. 2+3
- 5. Define a register. Construct a 4-bit serial-in-serial-out shift register using D-type flip-flops and explain its operation. 1+1+3

Section-III

Answer any *one* question: 10X1=10

- 6. What is a flip-flop? Briefly discuss the action of a delayed flip-flop. Explain the principle of operation of a J-K flip-flop. What do mean by race around condition? 1+3+5+1
- 7. Distinguish between series and parallel counter. What is the main advantage of a synchronous counter over a ripple counter? Draw the block diagram of an asynchronous counter and explain its operation. Show that this counter can also be used as a frequency divider. 2+1+5+2